

## Electricity - Notes

[Notes](#) [Previous Years Questions](#) [Important Questions](#)

### Electricity - Notes


**Charge(Q):-** The fundamental particle of an atom is called charge.

- It can be positive or negative.
- S.I. unit - **Coulomb (C)**

**Quantisation of Charge:-** Every charge is an integral multiple of a basic charge i.e., charge on an electron( $e^-$ ).

- **$Q=ne$**
- Number of electrons( $n$ ) =  $Q/e$
- Charge on an electron ( $1e^-$ ) =  $1.6 \times 10^{-19}$  C

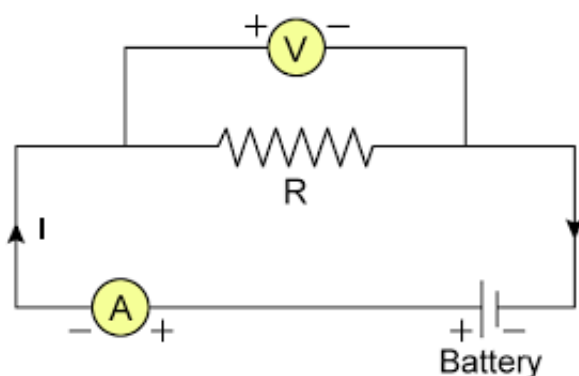**Electric Circuit:-** A continuous and closed path of an electric current is called an electric circuit.



**Electric current(I):-** The rate of flow of electric charge is called electric current.

- $I = Q/t$
- S.I. unit:- **Ampere(A)**
- Conventionally, the direction of flow of electric current is opposite to the direction of flow of electrons
- The amount of electric current in a circuit is measured by an instrument called **ammeter**.
- An ammeter is always connected in **series** in a circuit.
- $1 \text{ mA} = 10^{-3} \text{ A}$  &  $1 \text{ } \mu\text{A} = 10^{-6} \text{ A}$

**1 Ampere:-** The electric current flowing through a circuit is said to be 1 ampere when 1 coulomb of charge flows through it per second.

**Electric Potential:-** The work done to move a unit charge from infinity to a point is known as electric potential of that point.

**Electric Potential Difference:-** The work done to move a unit charge from one point to another point is called potential difference between the two points.

- $V = W/Q$
- S.I. unit:- **Volt(V)**
- Potential difference is measured by an instrument called **voltmeter**.
- Voltmeter is always connected in **parallel** across the points between which the potential difference is to be measured.

**1 Volt:-** The potential difference across the two points of a conductor is said to be 1 volt when 1 joule of work is done to move a charge from one point to the other.


**Ohm's Law:-** At constant temperature, the potential difference across the ends of a conductor is directly proportional to the amount of current flowing through it.

Mathematically,

V ? I

$V = IR$  where, R is constant of proportionality & is known as resistance.

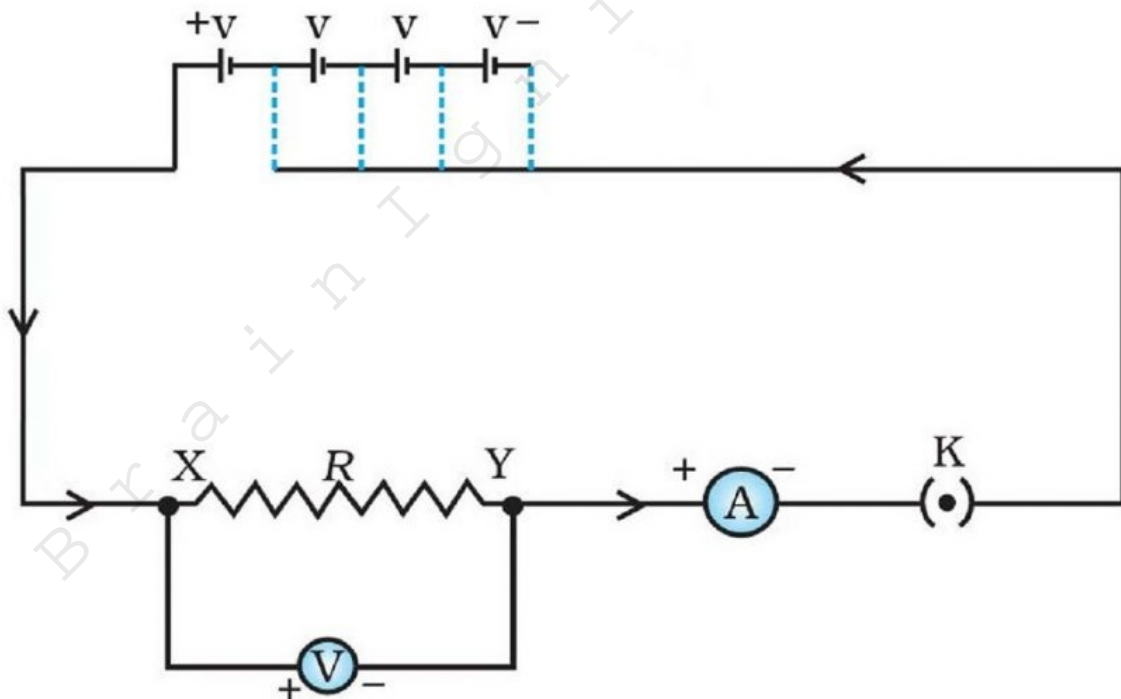**Circuit diagram and V-I graph for Ohm's law:-**



**Resistance:-** The property of a conductor to oppose the flow of charges through it is called resistance.

- $R = V/I$
- S.I. unit:- Ohm (?)

**1 Ohm:-** The resistance of a conductor is said to be 1  $\Omega$  if the potential difference across the ends of a conductor is 1 V and the current flowing through it is 1 A.

**Resistor:-** A conductor having some appreciable resistance

**Variable Resistance/Rheostat:-** A component used to regulate current without changing the voltage source

**Factors on which resistance of a conductor depends are:-**

- its length (l)
- its cross-section area (A)
- nature of its material

Mathematically,

$$R \propto l \text{ -----(i)}$$

$$R \propto 1/A \text{ -----(ii)}$$

On combining (i) & (ii):-


$R = \rho l / A$  where,  $\rho$  (rho) is constant of proportionality & is known as resistivity

**Resistivity/Specific Resistance(?):-** The resistance of the conductor of unit length & unit area of cross section is called its resistivity.

- $\rho = RA/l$
- S.I. unit :- ohm meter ( $\Omega \text{ m}$ )

**Resistors In Series:-** When two or more resistors are connected end to end to each other, then they are said to be connected in series. In series combination,

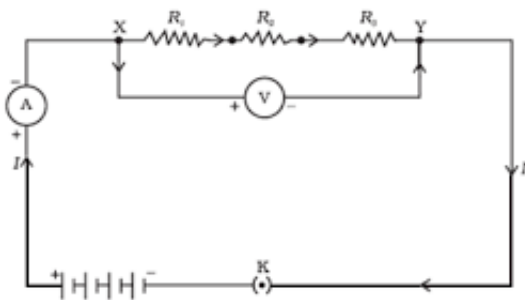- current flowing is same through each resistor.
- the potential difference across each resistor is different.



Resistors in series

Figure 3

Consider current 'I' is flowing through the circuit & the potential difference across resistors  $R_1$ ,  $R_2$  &  $R_3$  be  $V_1$ ,  $V_2$ ,  $V_3$  respectively. Let the total potential difference be 'V' & equivalent resistance be ' $R_s$ '.

On applying Ohm's law,

$$V = IR_s ; V_1 = IR_1 ; V_2 = IR_2 ; V_3 = IR_3$$


$$\text{Now, } V = V_1 + V_2 + V_3$$

$$\text{or, } IR_s = IR_1 + IR_2 + IR_3$$

$$\text{or, } R_s = R_1 + R_2 + R_3$$

**Resistors In Parallel:-** When two or more resistors are connected together between two points then they are said to be connected in parallel. In parallel combination,

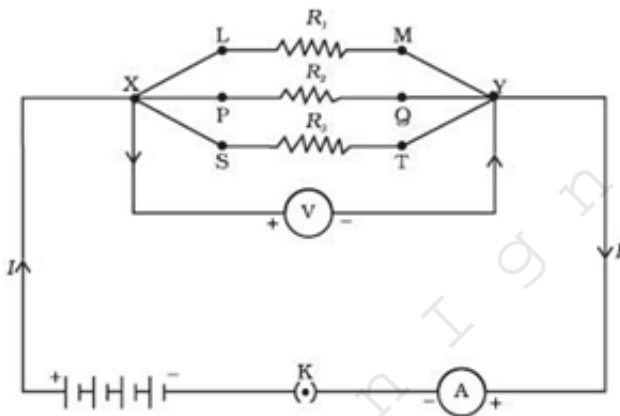- The potential difference is same across each resistor.
- The current flowing through each resistor is different.



Consider potential difference across the resistors be  $V$  & the current flowing through resistors  $R_1$ ,  $R_2$  &  $R_3$  be  $I_1$ ,  $I_2$  &  $I_3$  respectively. Let the total current flowing through the circuit be  $I$  & equivalent resistance be  $R_p$ .

By Ohm's law,

$$I = V/R_p ; I_1 = V/R_1 ; I_2 = V/R_2 ; I_3 = V/R_3$$

$$\text{Now, } I = I_1 + I_2 + I_3$$

$$\text{or, } V/R_p = V/R_1 + V/R_2 + V/R_3$$

$$\text{or, } 1/R_p = 1/R_1 + 1/R_2 + 1/R_3$$

**Electric Power:-** The amount of electrical energy consumed per unit time in an electric circuit is known as electric power.

$$P = W/t$$

$$\text{or } P = VQ/t$$

$$\text{or } P = VI = I^2R = V^2/R$$

- S.I. unit of power:- **Watt(W)**

**1 Watt:-** Electric power of an appliance is said to be 1 W if 1 A of current flows through it and the potential difference across its ends is 1 V.

**Heating Effect of Electric Current:-**

$$W = VQ = VIt$$

$$\text{or } H = VIt = I^2Rt$$

**Joule's Law of Heating:-** According to Joule's law of heating, heat produced in a resistor is directly proportional to

- square of current ( $H \propto I^2$ )
- resistance ( $H \propto R$ )

- time for which current flows (H ? t)

$$H = I^2Rt$$

**Practical Applications of Heating Effect of Electric Current:-** Appliances based on heating effect of electric current are **electric bulb, electric iron, electric toaster, electric oven, electric kettle, electric heater, fuse** etc.

- S.I. unit of energy:- **Joule(J)**
- Commercial unit of energy:- **kilowatt hour(kW h)**

**Conversion of Commercial Unit of Energy to S.I. Unit:-**

$$1 \text{ kW h} = 1000 \text{ W} \times 3600 \text{ s} = 3.6 \times 10^6 \text{ Ws} = 3.6 \times 10^6 \text{ J}$$

$$1 \text{ unit} = 1 \text{ kW h} = 3.6 \times 10^6 \text{ J}$$