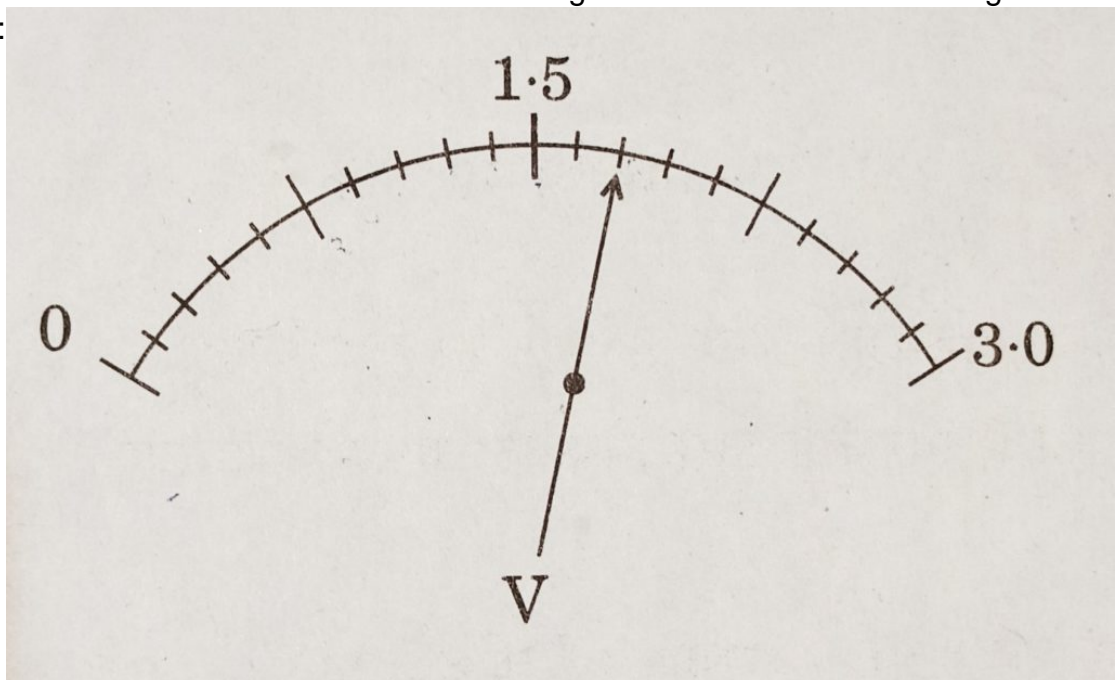


Electricity - Previous Years Questions

[Previous Years Questions](#) [Notes](#) [Important Questions](#)

Electricity - Previous Years Questions

1. Define 1 kilowatt hour. [1 mark] [CBSE 2019]
2. The values of mA and μ A are: [1 mark] [CBSE 2020]
 1. 10^{-6} A and 10^{-9} A respectively
 2. 10^{-3} A and 10^{-6} A respectively
 3. 10^{-3} A and 10^{-9} A respectively
 4. 10^{-6} A and 10^{-3} A respectively
3. A cylindrical conductor of length 'l' and uniform area of cross-section 'A' has resistance 'R'. Another conductor of length 2.5 l and resistance 0.5 R of the same material has area of cross-section: [1 mark] [CBSE 2020]
 1. 5 A
 2. 2.5 A
 3. 0.5 A
 4. 1/5 A
4. Define the term electrical resistivity of a material. [1 mark] [CBSE 2019]
5. Consider the scale of a voltmeter shown in the diagram and answer the following questions:



1. What is the least count of the voltmeter?
2. What is the reading shown by the voltmeter?
3. If this voltmeter is connected across a resistor of 20 Ω , how much current is

flowing through the resistor. **[2 marks] [CBSE 2019]**

6. The values of current (I) flowing through a given resistor (R), for the corresponding values of potential difference (V) across the resistor are as given below :

V(volts)	0.5	1.0	1.5	2.0	2.5	3.0	4.0	5.0
I(Ampere)	0.1	0.2	0.3	0.4	0.5	0.6	0.8	1.0

Plot a graph between current (I) and potential difference (V) and determine the resistance (R) of the resistor. **[2 marks] [CBSE 2018]**

7. Show how would you join three resistors each of resistance 9 Ω so that the equivalent resistance of the combination is (i) 13.5 Ω ? (ii) 6 Ω ?? **[3 marks] [CBSE 2018]**

8. a. Write Joule's law of heating.

b. Two lamps, one rated 100 W; 220 V, and the other 60 W; 220 V, are connected in parallel to electric mains supply. Find the current drawn by two bulbs from the line, if the supply voltage is 220 V. **[3 marks] [CBSE 2018]**

9. a. List the factors on which the resistance of a conductor in the shape of a wire depends.

b. Why are metals good conductor of electricity whereas glass is a bad conductor of electricity ? Give reason.

c. Why are alloys commonly used in electrical heating devices? Give reason. **[CBSE 2018] [3 Marks]**

10. a. Three resistors of resistances R_1 , R_2 & R_3 are connected (i) in series, & (ii) in parallel. Write expressions for the equivalent resistance of the combination in each case.

b. Two identical resistors of 12 Ω each are connected to a battery of 3 V. Calculate the ratio of the power consumed by the resulting combinations with minimum resistance & maximum resistance. **[CBSE 2019] [5 Marks]**

11. a. Write the relation between resistance & electrical resistivity of the material of a conductor in the shape of a cylinder of length 'l' & area of cross section 'A'. Hence derive the S.I. unit of electrical resistivity.

b. Resistance of a metal wire of length 5 m is 100 Ω . If the area of cross section of the wire is $3 \times 10^{-7} \text{ m}^2$, calculate the resistivity of the metal. **[CBSE 2019] [5 Marks]**

12. a. Two lamps rated 100 W, 220 V & 10 W, 220 V are connected in parallel to 220 V supply, calculate the total current through the circuit.

b. Two resistors x & y of resistances 2 Ω & 3 Ω respectively are first joined in parallel & then in series. In each case the voltage supplied is 5 V.

(i) Draw circuit diagrams to show the combination of resistors in each case.

(ii) Calculate the voltage across the 3 Ω resistor in the series combination of resistors. **[CBSE 2020] [5 Marks]**

13. a. State ohm's law.

b. How is an ammeter connected in an electric circuit?

c. The power of a lamp is 100 W. Find the energy consumed by it in 1 minute.

d. A wire of resistance 5 Ω is bent in the form of a closed circle. Find the resistance between two points at the ends of any diameter of the circle. **[5 marks] [CBSE 2020]**